

**American International University-Bangladesh (AIUB)**  
**Engineering Faculty**  
**EEE 2101: Electrical Circuits-2 (AC)**

**Assignment: Marks Distribution System**

	With in December 16, 2016	With in December 24, 2016	With in December 27, 2016	After December 27, 2016
<b>Parallel Resonance Circuit</b>	4	3	2	0
<b>Network Theorem</b>	4	3	2	0
<b>Polyphase Balance and Unbalanced System and Power Measurement</b>	8	6	4	0
<b>Couple Circuit</b>	4	3	2	0
<b>Total Marks</b>	<b>20</b>	<b>15</b>		<b>0</b>

### Parallel Resonance Circuit

[Q1] For a practical parallel resonance circuit write the express of followings: (i) Condition for parallel resonance in terms of susceptance, (ii) Condition for parallel resonance in terms of reactance, (iii) Resonance frequency, (iv) Quality factor, and (v) Bandwidth

[Q2] For a wave-trap circuit write the express of followings: (i) Condition for parallel resonance in terms of susceptance, (ii) Condition for parallel resonance in terms of reactance, (iii) Resonance frequency, (iv) Quality factor, and (v) Bandwidth


[P1] Two impedances  $Z_L = R_L + j14$  ohm and  $Z_C = 8.54 - j6.83$  ohm are connected in parallel. Calculate the value of  $R_L$  to make this circuit is resonance.

[P2] Two impedances  $Z_L = 4 + j14$  ohm and  $Z_C = -jX_C$  ohm are connected in parallel. Calculate the value of  $C$  to make this circuit is resonance at 1 kHz.

[P3] Two impedances  $Z_L = 4 + jX_L$  ohm and  $Z_C = 8.54 - j6.83$  ohm are connected in parallel. Calculate the value of  $L$  to make this circuit is resonance at 1 kHz.

[P4] A  $RL$  series branch having  $R_L = 7$  ohm and  $L = 2.23$  mH are connected with a  $RC$  series branch having  $R_C = 8.54$  ohm and  $C = 23.3$   $\mu$ F. Calculate (i) the resonance frequency, (ii) the quality factor, and (iii) the bandwidth.

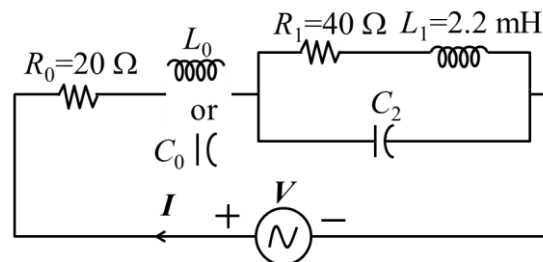[P5] Design a resonance circuit as shown in the following figure to pass any wave of 15 kHz and block 45 kHz wave. (i) Find the value of  $C_2$ . (ii) What type of reactance (inductive or capacitive) must be placed in series with the source? (iii) Calculate the value of  $L_0$  or  $C_0$  which is required to put. (iv) Calculate the impedance and current if the circuit is impressed by 200 V.




## Network Theorem


[Q1] State the Maximum Power Transfer Theorem. Write the expression of load impedance in terms of Thevenin's impedance to receive the maximum power by load impedance.

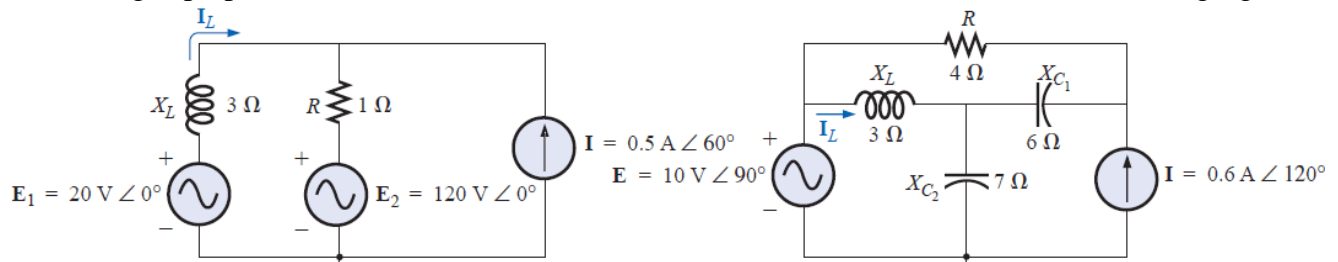[Q2] State the Super Position Theorem.

[P1] Using superposition, determine the current  $I_L$  for each network as shown in the following figure.



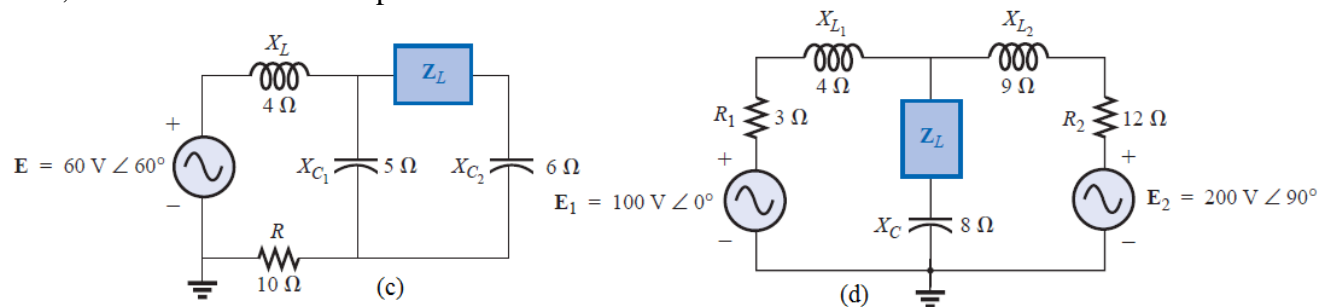[P2] Find the load impedance  $Z_L$  for the networks of following figures for maximum power to the load, and find the maximum power to the load.



## Polyphase Balanced System

[P1] If the line current is 120 A and line voltage is 440 V for a balanced five-phase system, find the magnitude of the phase voltage and the phase current for (i) the star-connection, and (ii) the mesh-connection.

[P2] A three-phase Y-connected balanced source with  $abc$  sequence is connected with a Y-connected balanced load having the per phase impedance  $10+j20 \Omega$ . The neutrals of both source and load are connected. The phase voltage of source is given by  $E_{an}=250\angle 0^\circ$  V. Calculate (i) the phase voltages ( $V_{an}$ ,  $V_{bn}$ ,  $V_{cn}$ ), (ii) the line voltages ( $E_{AB}$ ,  $E_{BC}$ ,  $E_{CA}$ ), (iii) the phase currents ( $I_{an}$ ,  $I_{bn}$ ,  $I_{cn}$ ), (iv) the line currents ( $I_{Aa}$ ,  $I_{Bb}$ ,  $I_{Cc}$ ), (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

[P3] A three-phase  $\Delta$ -connected balanced source with  $abc$  sequence is connected with a  $\Delta$ -connected balanced load. In each phase, a 20 ohm resistance is connected in parallel with a capacitor having 15 ohm reactance. The phase voltage of source is given by  $E_{AB}=220\angle 0^\circ$  V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.


[P4] A three-phase Y-connected balanced source with  $abc$  sequence is connected with a  $\Delta$ -connected balanced load having the per phase impedance  $12-j9 \Omega$ . The phase voltage of source is given by  $E_{an}=200\angle 0^\circ$  V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.

[P5] A three-phase  $\Delta$ -connected balanced source with  $abc$  sequence is connected with a Y-connected balanced load having the per-phase impedance  $3+j4 \text{ ohm}$ . The phase voltage of source is given by  $E_{AB}=110\angle 0^\circ$  V. Calculate (i) the phase voltage, (ii) the line voltage, (iii) the phase current, (iv) the line current, (v) the power factor and reactive factor, and (vi) the power, reactive power and apparent power.


[P6] A three-phase motor takes 10 kW to 0.7 power factor lagging from a source of 440 volts. It is in parallel with a balanced delta load having 18 ohms resistance and 24 ohms inductive reactance in series in each phase. Find the total volt-amperes, power, line current and power factor of the combination.
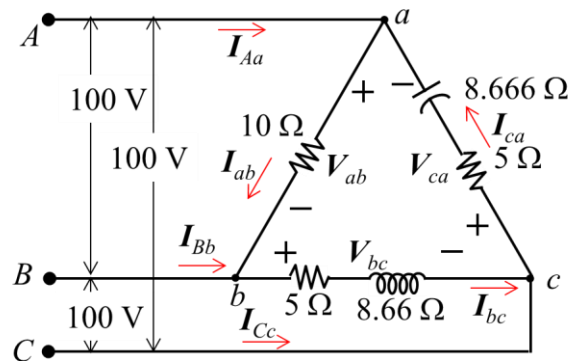
## Polyphase Unbalanced System


[P1] A balanced three-phase source of 100 V is connected with an unbalanced  $\Delta$ -connected load as shown in the following figure. Calculate (i) the phase currents ( $I_{ab}$ ,  $I_{bc}$ ,  $I_{ca}$ ), (ii) the line currents ( $I_{Aa}$ ,  $I_{Bb}$ ,  $I_{Cc}$ ), (iii) the overall power, reactive power, apparent power.



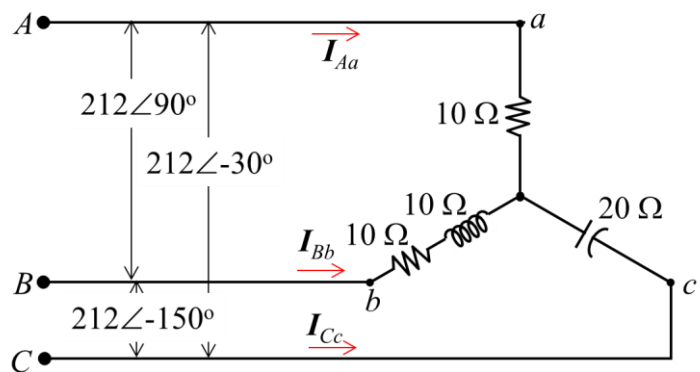[P2] A balanced three-phase source of 212 V is connected with an unbalanced Y-connected load as shown in the following figure. Calculate (i) the line currents ( $I_{Aa}$ ,  $I_{Bb}$ ,  $I_{Cc}$ ), and (ii) the overall power, reactive power, apparent power.



[P3] Refer to the following figure,  $E_{AN}$ ,  $E_{BN}$ , and  $E_{CN}$  are balanced three-phase voltages with magnitude of 115.4 volts and a phase sequence the sequence of ABC. Calculate (i) the phase voltages of load ( $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$ ), (ii) the phase currents of load ( $I_{ab}$ ,  $I_{bc}$ ,  $I_{ca}$ ), (iii) the line currents ( $I_{Aa}$ ,  $I_{Bb}$ ,  $I_{Cc}$ ). (iv) the total power, reactive power, and apparent power.

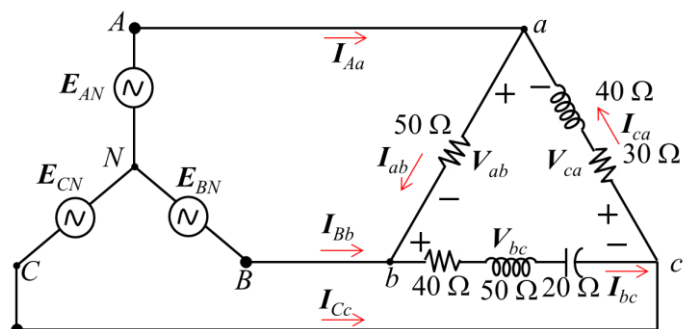

## Power Measurement of Polyphase System

[Q1] With vector diagram by using the two wattmeter method the measured power is given by:  $(\sqrt{3})V_L I_L \cos \theta$ .

[Q2] Draw the power factor vs watt-ratio curve.

[P1] The two wattmeter method produces wattmeter readings are 1560 W and 2100 W when connected to balanced delta-connected load. If the line voltage is 220 V, calculate (i) the per-phase power, (ii) the per-phase reactive power, (iii) the power factor, and (iv) the phase impedance.

[P2] Let the line voltage 208 V and the wattmeter readings of the balanced system are -560 W and 800 W. Determine (i) the total power, (ii) the total reactive power, (iii) the power factor, (iv) the phase impedance, and (v) Is the impedance inductive or capacitive.


[P2] For the unbalanced delta-connected load of following figures with two properly connected wattmeters: (i) Determine the magnitude and angle of the phase currents. (ii) Calculate the magnitude and angle of the line currents. (iii) Determine the power reading of each wattmeter. (iv) Calculate the total power absorbed by the load. (v) Compare the result of part (iv) with the total power calculated using the phase currents and the resistive elements.

## Coupling Circuit


[P1] Two similar coils have a coupling coefficient of 0.25. When they are connected cumulatively in series, the total inductance is 80 mH. Calculate the self-inductance inductance of each coil. Also, calculate the total inductance when the coils are differentially connected in series.

[P2] Two inductively coupled coils have self-inductances 7.5 H and 25 H. If the coupling coefficient is 0.8 (i) find the value of mutual inductance between the coils, and (ii) what is the maximum possible mutual inductance?

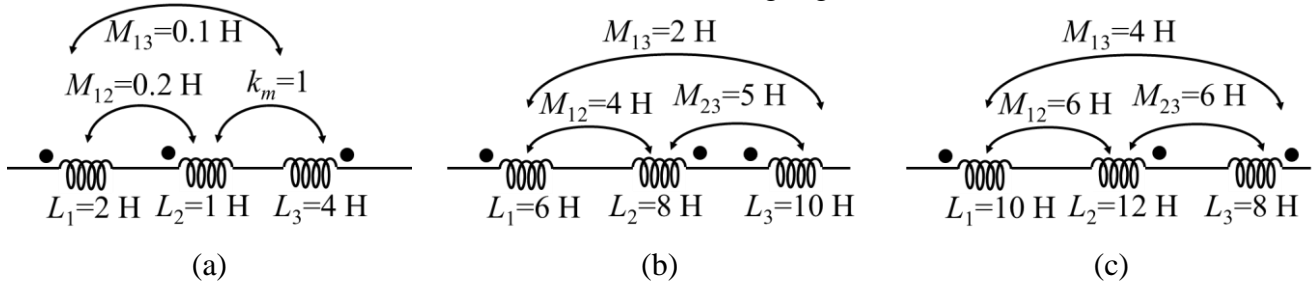
[P3] Find the total inductance of the series coils of following Figures.



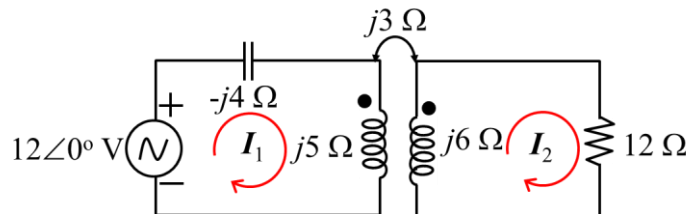[P4] For the following circuits write the loop equations and calculate (i) the currents,  $I_1$ , and  $I_2$ , and (ii) the equivalent impedance, and (iii) the consumed power.



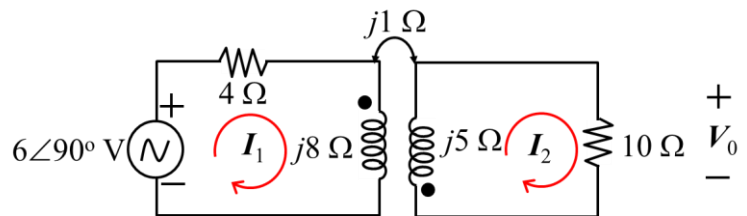[P5] For the following circuits write the loop equations and calculate (i) the currents,  $I_1$ ,  $I_2$ , and  $V_0$ , and (ii) the equivalent impedance, and (iii) the consumed power.



[P6] For the following circuits write the loop equations and calculate (i) the currents,  $I_1$ , and  $I_2$ , and (ii) the equivalent impedance, and (iii) the consumed power.

